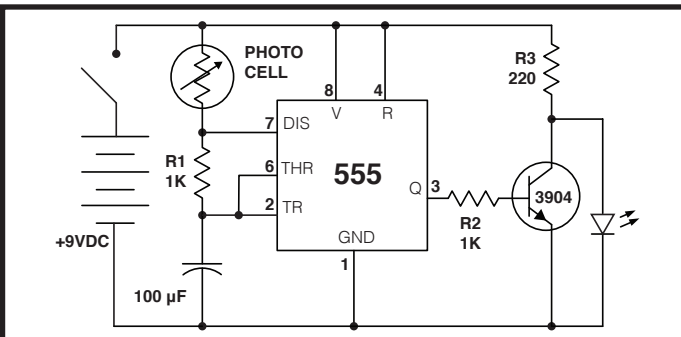



Building a Blinky Circuit!

BY JODY CULKIN & **Make:**
makezine.com


WE'RE GOING TO BUILD A SIMPLE PHOTOMETER USING A PHOTORESISTOR AND AN LED. THE MORE LIGHT FALLS ON THE PHOTORESISTOR, THE FASTER THE LED FLASHES.




HERE IS THE SCHEMATIC.

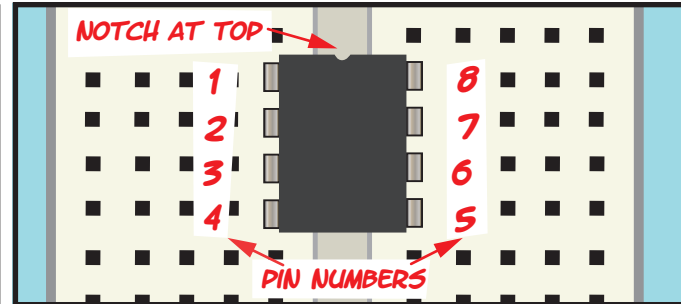

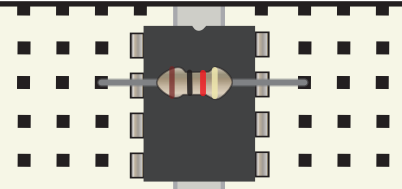
FIRST PUT THE 555 TIMER IC ACROSS THE TRENCH RIGHT IN THE MIDDLE OF THE BOARD.



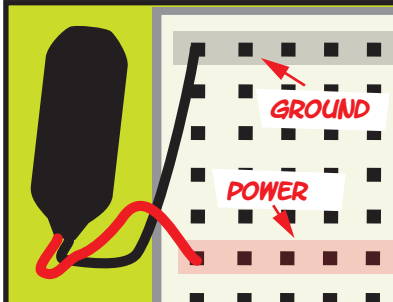
ATTACH A 1K RESISTOR ACROSS THE IC, BRIDGING PINS 2 AND 7. TRIM AND BEND COMPONENT LEADS, AS YOU GO, TO KEEP EVERYTHING COMPACT.




ATTACH THE BATTERY CLIP.

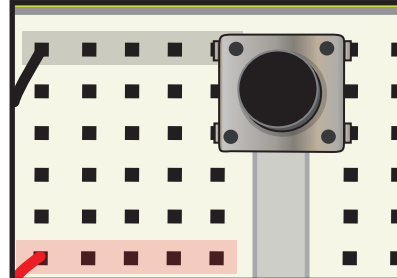

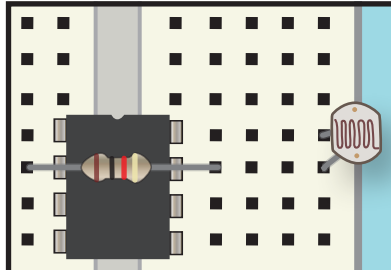
ATTACH A MOMENTARY SWITCH TO GROUND AT THE TOP OF THE BOARD.



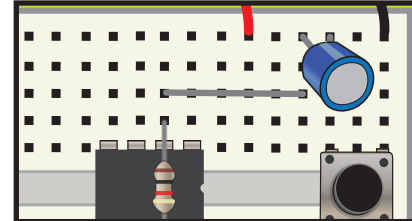
THE PHOTORESISTOR IS CONNECTED TO PIN 7 AND 8.



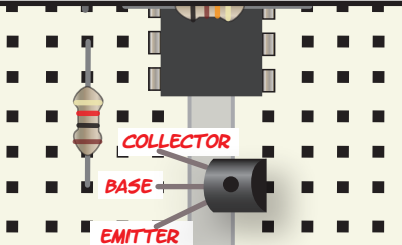
INSERT A 100UF CAPACITOR CONNECTING THE NEGATIVE LEAD TO THE SWITCH, AS SHOWN. JUMPER THE OTHER LEAD TO 555 PIN 2.



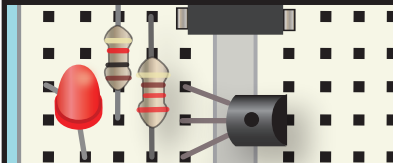
PLACE THE NPN TRANSISTOR BENEATH THE IC. PUT A 1K RESISTOR BETWEEN PIN 3 AND THE TRANSISTOR BASE.



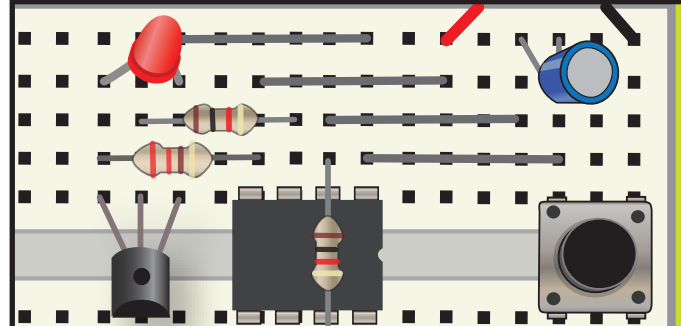
CONNECT THE LED'S ANODE TO THE TRANSISTOR'S EMITTER, AND ITS CATHODE TO THE COLLECTOR. CONNECT A 220(OHM) RESISTOR ACROSS THE EMITTER AND 555 PIN 4.




INSERT JUMPERS TO POWER AND GROUND.

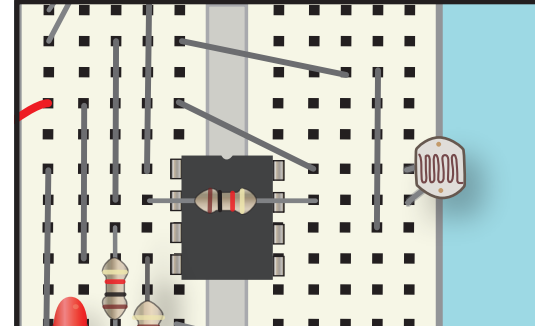

INSERT THESE JUMPERS AS SHOWN.

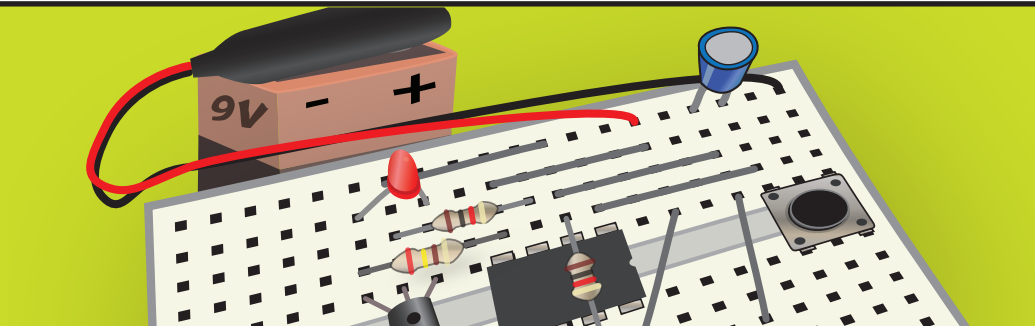

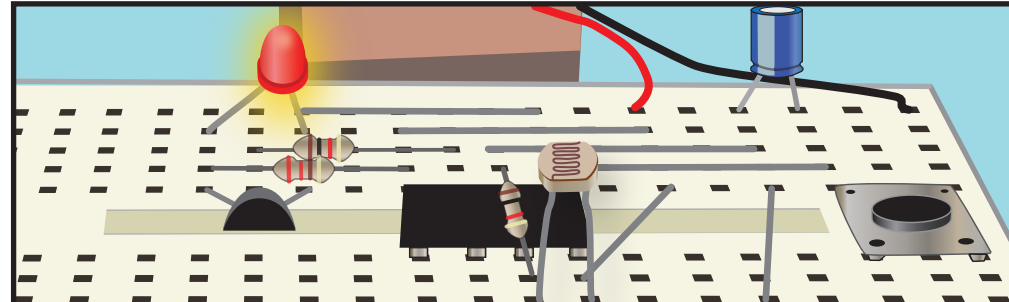ATTACH A 9 VOLT BATTERY TO THE BATTERY CLIP.



NOW, THE LED WILL FLASH MORE FREQUENTLY WHEN THERE IS A LOT OF LIGHT, LESS FREQUENTLY WHEN THE ROOM IS DIMMER.